

Step 14.

Recalculate D_{MAX} for continuous mode of operation from V_{MIN} and V_{OR} .

- Start continuous mode design.
- Recalculate D_{MAX} as:

$$D_{MAX} = \frac{V_{OR}}{V_{OR} + V_{MIN}}$$

Step 15.

Calculate K_{RP} from V_{MIN} , P_O , η , I_p , and D_{MAX} .

- K_{RP} is the ratio between the primary ripple current I_R and primary peak current I_p . And I_p is 90% of minimum I_{LIMIT} .

• From AN-16,
$$I_p = \frac{I_{AVG}}{\left(1 - \frac{K_{RP}}{2}\right) \times D_{MAX}}$$

and
$$I_{AVG} = \frac{P_O}{\eta \times V_{MIN}}$$

- By combining the above equations, K_{RP} can be expressed as:

$$K_{RP} = \frac{2 \times (I_p \times D_{MAX} \times \eta \times V_{MIN} - P_O)}{I_p \times D_{MAX} \times \eta \times V_{MIN}}$$

Step 16A, B, C.

Check K_{RP} against 0.6.

- $K_{RP} \geq 0.6$, go to Step 17B.
- $K_{RP} < 0.6$, set $K_{RP} = 0.6$.
 - Recalculate D_{MAX} using Step 15 equation.
 - Recalculate V_{OR} using Step 14 equation.
 - If $V_{OR} < 150$ V, go to Step 17B.
 - If $V_{OR} > 150$ V, go back to Step 7 and select higher current *TinySwitch*.

Step 17A, B.

Calculate primary inductance L_p .

- **Discontinuous mode:**

$$L_p = \frac{10^6 \times P_O}{\frac{1}{2} \times \frac{1}{0.9} \times I_p^2 \times f_s} \times \frac{Z \times (1 - \eta) + \eta}{\eta}$$

- **Continuous mode:**

$$L_p = \frac{10^6 \times P_O}{K_{RP} \times \left(1 - \frac{K_{RP}}{2}\right) \times \frac{1}{0.9} \times I_p^2 \times f_s} \times \frac{Z \times (1 - \eta) + \eta}{\eta}$$

- I_p is 90% of minimum I_{LIMIT} from *TinySwitch* data sheet as previously defined in Step 8.
- f_s is minimum switching frequency from *TinySwitch* data sheet.
- Please note the cancellation effect between the over temperature variations of I_p and f_s resulting in the additional 1/0.9 term.
- Z is loss allocation factor. If $Z = 0$, all losses are on the primary side. If $Z = 1$, all losses are on the secondary side.
- Since output diode loss and clamp/snubber loss are both secondary losses, $Z = 1$ is a reasonable starting point.

Step 18.

Design Transformer.

- Calculate turns ratio N_p/N_s .

$$\frac{N_p}{N_s} = \frac{V_{OR}}{V_O + V_D}$$

- Selecting core and bobbin

- With triple insulated secondary wire and no margin winding, EE16 core is suitable for most *TinySwitch* applications.
- To accommodate margin winding, EEL16 core must be used.
- In below 2 W and/or space constrained applications, EE13 or EF13 cores with special bobbin meeting safety requirements may be used.

- Calculate primary and secondary number of turns for peak flux density (B_p) not to exceed 3000 gauss. Limit B_p to 2500 gauss for low audio noise designs. Use the lowest practical value of B_p for the greatest reduction in audio noise. See AN-24 for additional information.
- Calculate primary number of turns (N_p)

$$N_p = 100 \times I_p' \times \frac{L_p}{B_p \times A_e}$$

where I_p' equals to maximum I_{LIMIT}

Handwritten notes:
 $N_p = 77$
 $I_p = 0.588$ A
 $L_p = 959 \mu$ H
 $A_e = 0.23$
 $B_p = 3190$??

